
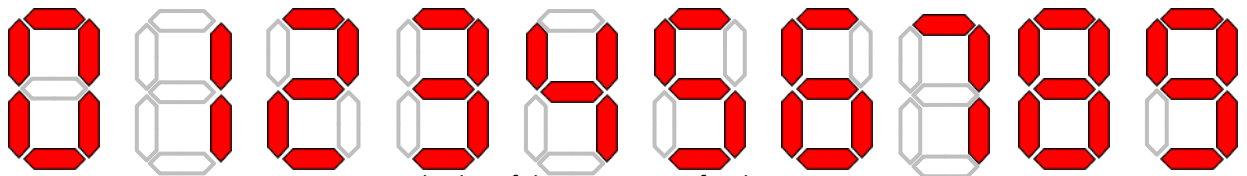


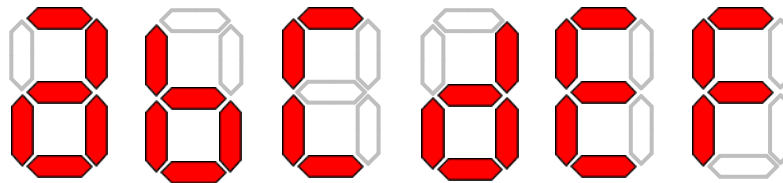**2020 Fall - ECE 2220 Laboratory 3****Binary Code Decimal, Hexadecimal Number Representation****1) Introduction**

In this lab the seven segment display (SSD) will be used to output the results of a 4-bit binary word in hexadecimal and then binary coded decimal output. A binary-coded-decimal (BCD) or a hexadecimal to SSD converter display is simply a combinational circuit with 4 binary inputs and 7 outputs. The 4-bit input is the BCD representation of digits 0-9 and the hexadecimal representation of digits 0-F and the. The 7-bit output is the state of each of SSD segments as shown in see in the figure below. Note the representation of some digits like 1, 6, and 9 might be different from one decoder to another.




Seven segment display of the BCD output for digits 0 to 9.



Seven segment display of the HEX output for digits 0 to F.

Seven-segment displays (SSD) are commonly found on computers, watches, VCRs, and other electronic devices to display numbers and characters. The seven-segment displays in the lab consist of seven Light Emitting Diodes (LEDs) in the configuration of a number “8”. Different segments can be illuminated to display different numbers and letters. The segments of a seven-segment display are illustrated in the figure below. The SSDs, in general, come in packages with either a common anode or a common cathode. The SSDs on the DE10 board are common-anode. In this format the LED turns on with negative logic – i.e. low.

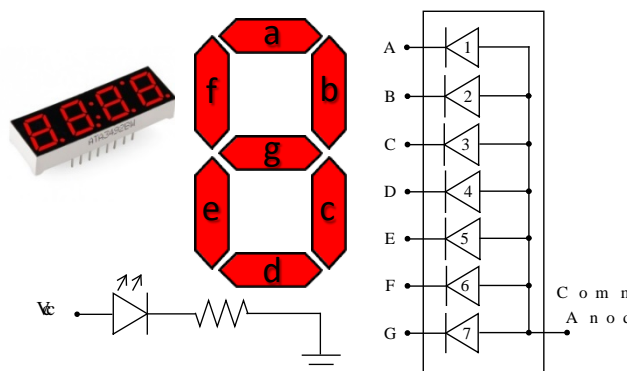

Common-anode SSD display

## 2020 Fall - ECE 2220 Laboratory 3


### Binary Code Decimal, Hexadecimal Number Representation

#### 2) Instructions

Take a 4 bit input from the switches SW[3], SW[2], SW[1], and SW[0]. Display the binary number as a BCD number on right most seven segment display HEX[0]. If the binary input number is greater than 9, the letter E should be displayed.

- a) Create a truth table and Karnaugh maps for the BCD-seven segment display

Decimal	BCD – input switches				Segment							
	s3	s2	s1	s0	LSB a	b	c	d	e	f	MSB g	
0	0	0	0	0	0	0	0	0	0	0	1	01
1	0	0	0	1	1	0	0	1	1	1	1	4F
2	0	0	1	0	0	0	1	0	0	1	0	12
3	0	0	1	1	0	0	0	0	1	1	0	06
4	0	1	0	0	1	0	0	1	1	0	0	4C
5	0	1	0	1	0	1	0	0	1	0	0	24
6	0	1	1	0	0	1	0	0	0	0	0	20
7	0	1	1	1	0	0	0	1	1	1	1	0F
8	1	0	0	0	0	0	0	0	0	0	0	00
9	1	0	0	1	0	0	0	0	1	0	0	04
10	1	0	1	0	0	1	1	0	0	0	0	30
11	1	0	1	1	0	1	1	0	0	0	0	30
12	1	1	0	0	0	1	1	0	0	0	0	30
13	1	1	0	1	0	1	1	0	0	0	0	30
14	1	1	1	0	0	1	1	0	0	0	0	30
15	1	1	1	1	0	1	1	0	0	0	0	30

 

1 var  $\rightarrow$  8 of 1s  
 2 vars  $\rightarrow$  4 of 1s  
 3 vars  $\rightarrow$  2 of 1s  
 4 vars  $\rightarrow$  1 of 1

AND  $\cdot$   
 OR  $+$

3

$S_1 S_0$

$S_3 S_2$	00	01	11	10
00	0	1	0	0
01	1	0	0	0
11	0	0	0	0
10	0	0	0	0

$$a = \underline{s_3' s_2' s_1' s_0 + s_3' s_2 s_1' s_0'}$$

**c**  $S_1 S_0$   $= s_3' s_1' (s_2' s_0 + s_2 s_0') = s_3' s_1' (s_2 \oplus s_0)$

$S_3 S_2$	00	01	11	10
00	0	0	0	1
01	0	0	0	0
11	1	1	1	1
10	0	0	1	1

$$c = \underline{s_3' s_2' s_1' s_0 + s_3 s_2 + s_3 s_1}$$

**e**  $S_1 S_0$

$S_3 S_2$	00	01	11	10
00	0	1	1	0
01	1	1	1	0
11	0	0	0	0
10	0	1	0	0

$$e = \underline{s_3' s_0 + s_3' s_2 s_1' s_0' + s_3 s_2' s_1' s_0}$$

**g**  $S_1 S_0$

$S_3 S_2$	00	01	11	10
00	1	1	0	0
01	0	0	1	0
11	0	0	0	0
10	0	0	0	0

$$g = \underline{s_3' s_2' s_1' + s_3' s_2 s_1 s_0}$$

**b**  $S_1 S_0$

$S_3 S_2$	00	01	11	10
00	0	0	0	0
01	0	1	0	1
11	1	1	1	1
10	0	0	1	1

$$b = \underline{s_3' s_2 s_1' s_0 + s_3' s_2 s_1 s_0' + s_3 s_2 + s_3 s_1}$$

$$= s_3' s_2 (s_1 \oplus s_0) + s_3 s_2 + s_3 s_1$$

$S_3 S_2$	00	01	11	10
00	0	1	0	0
01	1	0	1	0
11	0	0	0	0
10	0	0	0	0

$$d = \underline{s_3' s_2' s_1' s_0 + s_3' s_2 s_1' s_0' + s_3' s_2 s_1 s_0}$$

$$= s_3' s_1' (s_2 \oplus s_0) + s_3' s_2 s_1 s_0$$

**f**  $S_1 S_0$

$S_3 S_2$	00	01	11	10
00	0	1	1	1
01	0	0	1	0
11	0	0	0	0
10	0	0	0	0

$$f = \underline{s_3' s_2' s_0 + s_3' s_2' s_1 + s_3' s_1 s_0}$$

$$= s_3' s_2' (s_0 + s_1) + s_3' s_1 (s_2' + s_0)$$

- ✓ b) Create the Verilog code to perform this BCD function and output using simple combinational logic primitives (i.e. AND (&), OR (|), NOT (~) etc.) Compile your code and download it to the DE-10 board. *K-map a, b, c, d, e, f, g 7 cases*
- ✓ c) Re-write this code using a "case" statement. Compile your code and download it to the DE-10 board. *0-9, E 16 cases*
- ✓ d) Again using a case statement, re-write the code to display the hexadecimal representations of the input switches. Comment on the two Verilog implementations. *0-9, a-f*

### The Case Statement

The case statement compares an expression to a series of cases and executes the statement or statement group associated with the first matching case:

- case statement supports single or multiple statements.
- Group multiple statements using begin and end keywords.

Syntax of a case statement look as shown below.

```
case ()
< case1 > : < statement >
< case2 > : < statement >
.....
default : < statement >
endcase
```

#### Example- case

```
1 module mux (a,b,c,d,sel,y);
2 input a, b, c, d;
3 input [1:0] sel;
4 output y;
5
6 reg y;
7
8 always @ (a or b or c or d or sel)
9 case (sel)
10 0: y = a;
11 1: y = b;
12 2: y = c;
13 3: y = d;
14 default: $display("Error in SEL");
15 endcase
16
17 endmodule
```

#### Example- case without default

```
1 module mux_without_default (a,b,c,d,sel,y);
2 input a, b, c, d;
3 input [1:0] sel;
4 output y;
5
6 reg y;
7
8 always @ (a or b or c or d or sel)
9 case (sel)
10 0: y = a;
11 1: y = b;
12 2: y = c;
13 3: y = d;
14 2'bxx,2'bx0,2'bx1,2'b0x,2'b1x,
15 2'bzz,2'bz0,2'bz1,2'b0z,2'b1z : $display("Error in SEL");
16 endcase
17
18 endmodule
```

The example above shows how to specify multiple case items as a single case item.

The Verilog case statement does an identity comparison (like the == operator); one can use the case statement to check for logic x and z values as shown in the example below.

#### ✦ Example- casez

```

1 module casez_example();
2 reg [3:0] opcode;
3 reg [1:0] a,b,c;
4 reg [1:0] out;
5
6 always @ (opcode or a or b or c)
7 casez(opcode)
8   4'b1zzx : begin // Don't care about lower 2:1 bit, bit 0 match with x
9               out = a;
10              $display("@%0dns 4'b1zzx is selected, opcode %b", $time, opcode);
11            end
12   4'b01?? : begin
13               out = b; // bit 1:0 is don't care
14              $display("@%0dns 4'b01?? is selected, opcode %b", $time, opcode);
15            end
16   4'b001? : begin // bit 0 is don't care
17               out = c;
18              $display("@%0dns 4'b001? is selected, opcode %b", $time, opcode);
19            end
20   default : begin
21              $display("@%0dns default is selected, opcode %b", $time, opcode);
22            end
23 endcase
24
25 // Testbench code goes here
26 always #2 a = $random;
27 always #2 b = $random;
28 always #2 c = $random;
29
30 initial begin
31   opcode = 0;
32   #2 opcode = 4'b101x;
33   #2 opcode = 4'b0101;
34   #2 opcode = 4'b0010;
35   #2 opcode = 4'b0000;
36   #2 $finish;
37 end
38
39 endmodule

```

#### ✦ Example- case with x and z

```

1 module case_xz(enable);
2 input enable;
3
4 always @ (enable)
5 case(enable)
6   1'bz : $display ("enable is floating");
7   1'bx : $display ("enable is unknown");
8   default : $display ("enable is %b", enable);
9 endcase
10
11 endmodule

```

You could download file case\_xz.v [here](#)

#### ❖ The casez and casex statement

Special versions of the case statement allow the x and z logic values to be used as "don't care":

- casez : Treats z as don't care.
- casex : Treats x and z as don't care.

# ✦ Example- casex

```

1 module casex_example();
2 reg [3:0] opcode;
3 reg [1:0] a,b,c;
4 reg [1:0] out;
5
6 always @ (opcode or a or b or c)
7 casex(opcode)
8   4'b1zzx : begin // Don't care 2:0 bits
9               out = a;
10              $display("@%0dns 4'b1zzx is selected, opcode %b", $time, opcode);
11            end
12   4'b01?? : begin // bit 1:0 is don't care
13               out = b;
14              $display("@%0dns 4'b01?? is selected, opcode %b", $time, opcode);
15            end
16   4'b001? : begin // bit 0 is don't care
17               out = c;
18              $display("@%0dns 4'b001? is selected, opcode %b", $time, opcode);
19            end
20   default : begin
21               $display("@%0dns default is selected, opcode %b", $time, opcode);
22            end
23 endcase
24
25 // Testbench code goes here
26 always #2 a = $random;
27 always #2 b = $random;
28 always #2 c = $random;
29
30 initial begin
31   opcode = 0;
32   #2 opcode = 4'b101x;
33   #2 opcode = 4'b0101;
34   #2 opcode = 4'b0010;
35   #2 opcode = 4'b0000;
36   #2 $finish;
37 end
38
39 endmodule

```

# ✦ Example- Comparing case, casex, casez

```

1 module case_compare;
2
3 reg sel;
4
5 initial begin
6   #1 $display ("\\n   Driving 0");
7   sel = 0;
8   #1 $display ("\\n   Driving 1");
9   sel = 1;
10  #1 $display ("\\n   Driving x");
11  sel = 1'bx;
12  #1 $display ("\\n   Driving z");
13  sel = 1'bz;
14  #1 $finish;
15 end
16
17 always @ (sel)
18 case (sel)
19   1'b0 : $display("Normal : Logic 0 on sel");
20   1'b1 : $display("Normal : Logic 1 on sel");
21   1'bx : $display("Normal : Logic x on sel");
22   1'bz : $display("Normal : Logic z on sel");
23 endcase
24
25 always @ (sel)
26 casex (sel)
27   1'b0 : $display("CASEX : Logic 0 on sel");
28   1'b1 : $display("CASEX : Logic 1 on sel");
29   1'bx : $display("CASEX : Logic x on sel");
30   1'bz : $display("CASEX : Logic z on sel");
31 endcase
32
33 always @ (sel)
34 casez (sel)
35   1'b0 : $display("CASEZ : Logic 0 on sel");
36   1'b1 : $display("CASEZ : Logic 1 on sel");
37   1'bx : $display("CASEZ : Logic x on sel");
38   1'bz : $display("CASEZ : Logic z on sel");
39 endcase
40
41 endmodule

```