

Latches & Flip-Flops



**University
of Manitoba**

Combination/Sequential circuits

- Combinational circuits
 - Uses primitive gates
- Sequential circuits
 - Uses primitive gates
 - Also uses feedback and memory elements
 - Latched and flip-flops
 - Have feedback and are a memory element
 - Can be asynchronous – not synchronized to a clock
 - Can be synchronous – synchronized to a clock

Latch


- Since latches are a memory with feedback
 - Always concerned with the
 - Present output or state Q_t
 - And the next output state Q_{t+1}
- Combinational circuits (what we have done so far)
 - Output only depends on the inputs
- Sequential circuits (with latches and flip flops)
 - Output depends on the inputs but also on the current state or current output values
- Many different kinds SR, D, JK, T etc,

SR Latch

- States (outputs) can be defined by a truth table

“Truth table” or “characteristic table”

S	R	Current State	Next State
		Q_t	Q_{t+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	?
1	1	1	?

 


S	R	Q_{t+1}
0	0	Q_t
0	1	0
1	0	1
1	1	0/1 ?

undefined state


Gated SR Latch (with clock)

 - States (outputs) can be defined by a truth table
- Clock – square wave, 50 % duty, at given frequency




Characteristic table

Clock	S	R	Q_{t+1}
0	x	x	Q_t
1	0	0	Q_t
1	0	0	0
1	0	1	1
1	1	1	0/1

 


Gated SR Latch - NAND (with clock)

 - Can also be done using just NAND gates
- Clock – square wave, 50 % duty, at given frequency



Characteristic table

Clock	S	R	Q_{t+1}
0	x	x	Q_t
1	0	0	Q_t
1	0	0	1
1	0	1	0
1	0	1	0

 

Gated D Latch (with clock)


- D-latch transfers input D to output Q

- Next state $Q_{t+1} = D$
- Simple 1-bit register (memory cell)
- From SR latch – but $R = \bar{S}$


Characteristic table

Clock	D	Q_{t+1}
0	X	Q_t
1	0	$0 = D$
1	1	$1 = D$

↳ when clock 's ON

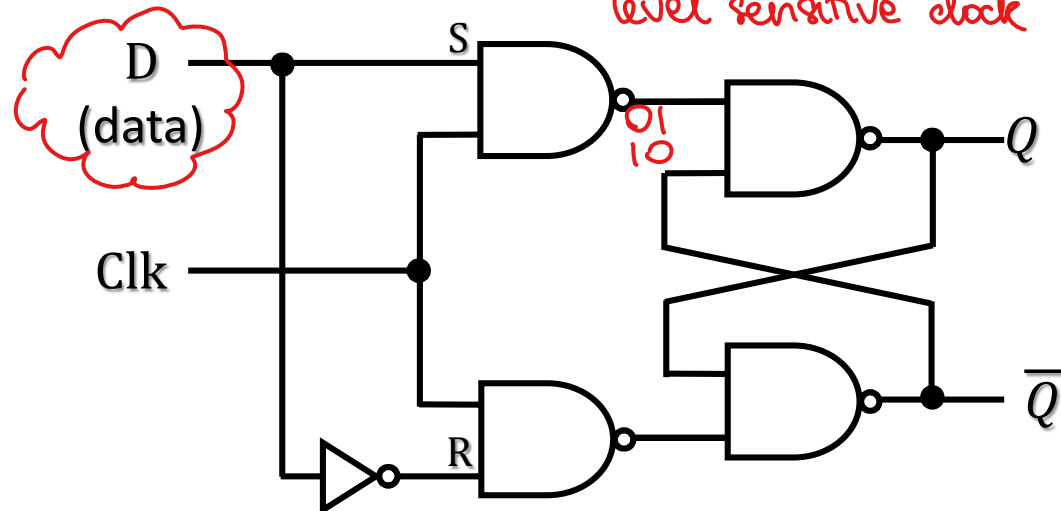

D-latch symbol

 

JK Latch *(SR + D + T 's functn)*





• JK-latch – likely most versatile latch

Characteristic table

Clock	J	K	Q_{t+1}
0	x	x	Q_t
1	0	0	Q_t
1	0	1	0
1	1	0	1
1	1	1	$\overline{Q_t}$

toggle output

JK-latch symbol

    


Make 1 latch from another type

- JK-latch – from a D
- Need to produce D as a function of J and K

What "D" input
produce this value

J	K	Q_t	Q_{t+1}	D
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	0
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0

toggle

 

		JK			
Q	D	00	01	11	10
		0	0	1	1
		1	0	0	1

$JQ + KQ$